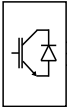


$V_{dc} = 600 \text{ V}$

0.5 MVA



$V_{ac} = 230 \text{ V}$

50 Hz



$T_{amb} = 25^{\circ}\text{C}$
Simulation period = 1 h

